

EVOX 2

400.2 EVOX2 - 4 Ω

Power @ 12.6V @ 2Ω: 2 X 200 WRMS
Power @ 12.6V @ 4Ω: 2 X 132 WRMS
Power @ 12.6V @ 1Ω: N/A
Bridge Power @ 12.6V @ 4Ω: 1 X 400 WRMS
Frequency Response: 5Hz – 22kHz



400.4 EVOX2 - 4 Ω

Power @ 12.6V @ 4Ω: 4 X 66 WRMS
Power @ 12.6V @ 2Ω: 4 X 100 WRMS
Power @ 12.6V @ 1Ω: N/A
Bridge Power @ 12.6V @ 4Ω: 2 X 200 WRMS
Bridge Power @ 12.6V @ 2Ω: N/A
Frequency Response: 5Hz – 22kHz

800.4 EVOX2 - 4 Ω

Power @ 12.6V @ 4Ω: 4 X 132 WRMS
Power @ 12.6V @ 2Ω: 4 X 200 WRMS
Power @ 12.6V @ 1Ω: N/A
Bridge Power @ 12.6V @ 4Ω: 2 X 400 WRMS
Bridge Power @ 12.6V @ 2Ω: N/A
Frequency Response: 5Hz – 22kHz



1200.2 EVOX2 - 2 Ω

Power @ 12.6V @ 4Ω: 2 X 261 WRMS
Power @ 12.6V @ 2Ω: 2 X 396 WRMS
Power @ 12.6V @ 1Ω: 2 X 600 WRMS
Bridge Power @ 12.6V @ 4Ω: 1 X 792 WRMS
Bridge Power @ 12.6V @ 2Ω: 1 X 1200 WRMS
Frequency Response: 5Hz – 22kHz



1200.2 EVOX2 - 4 Ω

Power @ 12.6V @ 4Ω: 2 X 396 WRMS
Power @ 12.6V @ 2Ω: 2 X 600 WRMS
Power @ 12.6V @ 1Ω: N/A
Bridge Power @ 12.6V @ 4Ω: 1 X 1200 WRMS
Bridge Power @ 12.6V @ 2Ω: N/A
Frequency Response: 5Hz – 22kHz

1200.4 EVOX2 - 2 Ω

Power @ 12.6V @ 4Ω: 4 X 130 WRMS
Power @ 12.6V @ 2Ω: 4 X 198 WRMS
Power @ 12.6V @ 1Ω: 4 X 300 WRMS
Bridge Power @ 12.6V @ 4Ω: 2 X 396 WRMS
Bridge Power @ 12.6V @ 2Ω: 2 X 600 WRMS
Frequency Response: 5Hz – 22kHz



1200.4 EVOX2 - 4 Ω

Power @ 12.6V @ 4Ω: 4 X 198 WRMS
Power @ 12.6V @ 2Ω: 4 X 300 WRMS
Power @ 12.6V @ 1Ω: N/A
Bridge Power @ 12.6V @ 4Ω: 2 X 600 WRMS
Bridge Power @ 12.6V @ 2Ω: N/A
Frequency Response: 5Hz – 22kHz

1600.1 EVOX2 - 1 Ω

Power @ 4Ω: 1 X 697 WRMS
Power @ 2Ω: 1 X 1056 WRMS
Power @ 1Ω: 1 X 1600 WRMS
Frequency Response: 5Hz – 25kHz



1600.1 EVOX2 - 2 Ω

Power @ 4Ω: 1 X 1056 WRMS
Power @ 2Ω: 1 X 1600 WRMS
Power @ 1Ω: N/A
Frequency Response: 5Hz – 25kHz

2400.4 EVOX2 - 2 Ω

Power @ 12.6V @ 4Ω: 4 X 261 WRMS
Power @ 12.6V @ 2Ω: 4 X 396 WRMS
Power @ 12.6V @ 1Ω: 4 X 600 WRMS
Bridge Power @ 12.6V @ 4Ω: 2 X 792 WRMS
Bridge Power @ 12.6V @ 2Ω: 2 X 1200 WRMS
Frequency Response: 5Hz – 22kHz



2400.4 EVOX2 - 4 Ω

Power @ 12.6V @ 4Ω: 4 X 396 WRMS
Power @ 12.6V @ 2Ω: 4 X 600 WRMS
Power @ 12.6V @ 1Ω: N/A
Bridge Power @ 12.6V @ 4Ω: 2 X 1200 WRMS
Bridge Power @ 12.6V @ 2Ω: N/A
Frequency Response: 5Hz – 22kHz

3000.1 EVOX2 - 1 Ω

Power @ 12.6V @ 4Ω: 1 X 1307 WRMS
Power @ 12.6V @ 2Ω: 1 X 1980 WRMS
Power @ 12.6V @ 1Ω: 1 X 3000 WRMS
Frequency Response: 5Hz – 25kHz



3000.1 EVOX2 - 2 Ω

Power @ 12.6V @ 4Ω: 1 X 1980 WRMS
Power @ 12.6V @ 2Ω: 1 X 3000 WRMS
Power @ 12.6V @ 1Ω: N/A
Frequency Response: 5Hz – 25kHz

5000.1 EVOX2 - 1 Ω

Power @ 12.6V @ 4Ω: 1 X 2178 WRMS
Power @ 12.6V @ 2Ω: 1 X 3300 WRMS
Power @ 12.6V @ 1Ω: 1 X 5000 WRMS
Frequency Response: 5Hz – 6kHz



5000.1 EVOX2 - 2 Ω

Power @ 12.6V @ 4Ω: 1 X 3300 WRMS
Power @ 12.6V @ 2Ω: 1 X 5000 WRMS
Power @ 12.6V @ 1Ω: N/A
Frequency Response: 5Hz – 6kHz

8000.1 EVOX2 - 1 Ω

Power @ 12.6V @ 4Ω: 1 X 3485 WRMS
Power @ 12.6V @ 2Ω: 1 X 5280 WRMS
Power @ 12.6V @ 1Ω: 1 X 8000 WRMS
Frequency Response: 5Hz – 6kHz



8000.1 EVOX2 - 2 Ω

Power @ 12.6V @ 4Ω: 1 X 5280 WRMS
Power @ 12.6V @ 2Ω: 1 X 8000 WRMS
Power @ 12.6V @ 1Ω: N/A
Frequency Response: 5Hz – 6kHz

12000.1 EVOX2 - 1 Ω

Power @ 12.6V @ 4Ω: 1 X 5227 WRMS
Power @ 12.6V @ 2Ω: 1 X 7920 WRMS
Power @ 12.6V @ 1Ω: 1 X 12000 WRMS
Frequency Response: 5Hz – 500 Hz



12000.1 EVOX2 - 2 Ω

Power @ 12.6V @ 4Ω: 1 X 7920 WRMS
Power @ 12.6V @ 2Ω: 1 X 12000 WRMS
Power @ 12.6V @ 1Ω: N/A
Frequency Response: 5Hz – 500 Hz



20000.1 EVOX2 - 1 Ω

Power @ 12.6V @ 4Ω: 1 X 8712 WRMS
Power @ 12.6V @ 2Ω: 1 X 13200 WRMS
Power @ 12.6V @ 1Ω: 1 X 20000 WRMS
Frequency Response: 5Hz – 500 Hz

35000.1 EVOX2 - 1 Ω

Power @ 12.6V @ 4Ω: 1 X 15246 WRMS
Power @ 12.6V @ 2Ω: 1 X 23100 WRMS
Power @ 12.6V @ 1Ω: 1 X 35000 WRMS
Frequency Response: 5Hz – 500 Hz
To be used only in SPL Competitions (Burr Only)!

SD RLC

Remote Level Control / Bass Knob
Compatible with: 3000.1/5000.1/8000.1/
12000.1/20000.1 and 35000.1 EVOX



EVOPS

800.1 EVOPS - 2 Ω

Power @ 12.6V @ 4 Ω : 1 X 528 WRMS

Power @ 12.6V @ 2 Ω : 1 X 800 WRMS

Power @ 12.6V @ 1 Ω : N/A

Frequency Response: 5Hz – 500 Hz

800.1 EVOPS - 4 Ω

Power @ 12.6V @ 4 Ω : 1 X 800 WRMS

Power @ 12.6V @ 2 Ω : N/A

Power @ 12.6V @ 1 Ω : N/A

Frequency Response: 5Hz – 500 Hz

800.4 EVOPS - 4 Ω

Power @ 12.6V @ 4 Ω : 4 X 132 WRMS

Power @ 12.6V @ 2 Ω : 4 X 200 WRMS

Power @ 12.6V @ 1 Ω : N/A

Bridge Power @ 12.6V @ 4 Ω : 2 X 400 WRMS

Bridge Power @ 12.6V @ 2 Ω : N/A

Frequency Response: 5Hz – 22kHz

1200.4 EVOPS - 2 Ω

Power @ 12.6V @ 4 Ω : 4 X 130 WRMS

Power @ 12.6V @ 2 Ω : 4 X 198 WRMS

Power @ 12.6V @ 1 Ω : 4 X 300 WRMS

Bridge Power @ 12.6V @ 4 Ω : 2 X 396 WRMS

Bridge Power @ 12.6V @ 2 Ω : 2 X 600 WRMS

Frequency Response: 5Hz – 22kHz

1200.4 EVOPS - 4 Ω

Power @ 12.6V @ 4 Ω : 4 X 198 WRMS

Power @ 12.6V @ 2 Ω : 4 X 300 WRMS

Power @ 12.6V @ 1 Ω : N/A

Bridge Power @ 12.6V @ 4 Ω : 2 X 600 WRMS

Bridge Power @ 12.6V @ 2 Ω : N/A

Frequency Response: 5Hz – 22kHz

2000.4 EVOPS - 2 Ω

Power @ 12.6V @ 4 Ω : 4 X 217 WRMS

Power @ 12.6V @ 2 Ω : 4 X 330 WRMS

Power @ 12.6V @ 1 Ω : 4 X 500 WRMS

Bridge Power @ 12.6V @ 4 Ω : 2 X 660 WRMS

Bridge Power @ 12.6V @ 2 Ω : 2 X 1000 WRMS

Frequency Response: 5Hz – 22kHz

2000.4 EVOPS - 4 Ω

Power @ 12.6V @ 4 Ω : 4 X 330 WRMS

Power @ 12.6V @ 2 Ω : 4 X 500 WRMS

Power @ 12.6V @ 1 Ω : N/A

Bridge Power @ 12.6V @ 4 Ω : 2 X 1000 WRMS

Bridge Power @ 12.6V @ 2 Ω : N/A

Frequency Response: 5Hz – 22kHz

